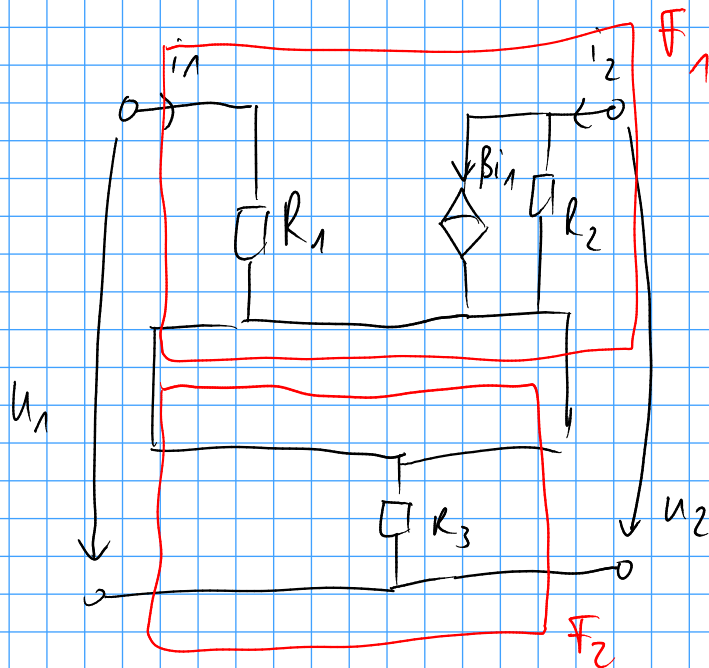



ST 1 - Tutorium - Blatt 6



$F_1 \rightarrow$ in Reihe verschaltet

$\rightarrow R_F = R_{F1} + R_{F2}$

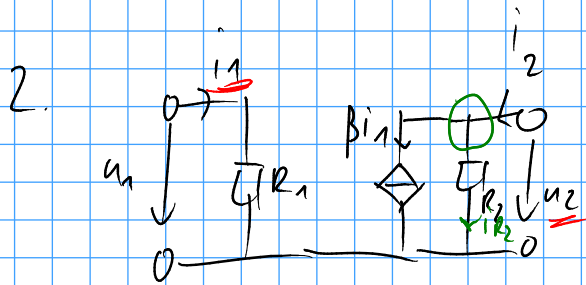1. Hybrid $\left\{ \begin{array}{l} \text{Reihen-Parallel} \\ \text{Parallel-Reihe} \end{array} \right.$ $H_{ges} = H_1 + H_2$
 $H'_{ges} = H'_1 + H'_2$



LL/KS-Methode:

$$\begin{pmatrix} u_1 \\ u_2 \end{pmatrix} = \begin{pmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix}$$

$$r_{11} = \frac{u_1}{i_1} \Big|_{i_2=0} = R_1$$

$$r_{12} = \frac{u_1}{i_2} \Big|_{i_1=0} = 0$$

$$r_{21} = \frac{u_2}{i_1} \Big|_{i_2=0} = -R_2\beta$$

$$r_{22} = \frac{u_2}{i_2} \Big|_{i_1=0} = R_2$$


KCL: $-i_2 + \beta i_1 + i_{R_2} = 0$

$i_{R_2} = i_2 - \beta i_1 \Big|_{i_2=0} = -\beta i_1$

$u_2 = R_2 i_{R_2} \Big|_{i_2=0} = -R_2 \beta i_1$

$\Rightarrow R_{F1} = \begin{pmatrix} R_1 & 0 \\ -R_2\beta & R_2 \end{pmatrix}$

F₂ :

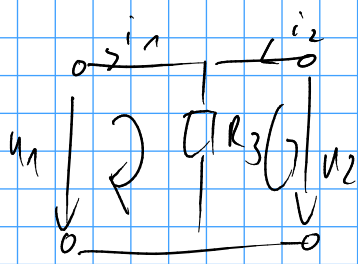

$$R_{F2} = \begin{pmatrix} R_3 & R_3 \\ R_3 & R_3 \end{pmatrix}$$

$$\tilde{R}_{ges} = \tilde{R}_1 + \tilde{R}_2 = \begin{pmatrix} R_1 + R_3 & R_3 \\ -R_2\beta + R_3 & R_2 + R_3 \end{pmatrix}$$

4. Kettenverschaltung: Kettenmatrix notwendig

$$\tilde{H} = \begin{pmatrix} 1 \Omega & -1 \\ 1 & 2S \end{pmatrix} \quad \det \tilde{H} = 2 + 1 = 3$$

$$\tilde{A} = \frac{1}{h_{21}} \begin{pmatrix} -\det H & -h_{11} \\ -h_{22} & -1 \end{pmatrix} = \frac{1}{1} \begin{pmatrix} -3 & -1 \Omega \\ -2S & -1 \end{pmatrix} = \begin{pmatrix} -3 & -1 \Omega \\ -2S & -1 \end{pmatrix}$$

$$\tilde{A}_F = \frac{1}{r_{21}} \begin{pmatrix} r_{11} & \det R \\ 1 & r_{22} \end{pmatrix} \quad \det \tilde{R} = R_1 R_2 + R_1 R_3 + R_2 R_3 (1 + \beta)$$

$$\Rightarrow \tilde{A}_F = \frac{1}{-R_2\beta + R_3} \begin{pmatrix} R_1 + R_3 & R_1 R_2 + R_1 R_3 + R_2 R_3 (1 + \beta) \\ 1 & R_2 + R_3 \end{pmatrix}$$


Multiplikation

$$\tilde{A}_{ges} = \tilde{A}_F \odot \tilde{A}_H = \frac{1}{-R_2\beta + R_3} \begin{pmatrix} -3(R_1 + R_3) - 2S(R_1 R_2 + R_1 R_3 + R_2 R_3 (1 + \beta)) & \cancel{+1} \\ -3 - 2S(R_2 + R_3) & \cancel{+1} \end{pmatrix} \begin{matrix} \cancel{+1} \\ v_2 \end{matrix}$$

$$\cancel{+1} \quad -1 \Omega (R_1 + R_3) - 1 (R_1 R_2 + R_1 R_3 + R_2 R_3 (1 + \beta))$$

$$\cancel{+1} \quad -2S - (R_2 + R_3)$$

Quiz

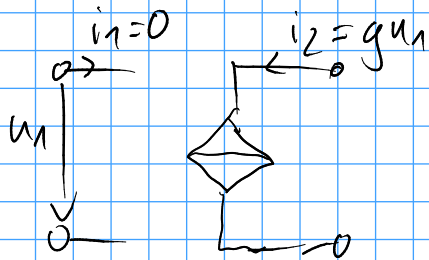

$$\begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = G \begin{pmatrix} u_1 \\ u_2 \end{pmatrix}$$

$$G = \begin{pmatrix} 0 & 0 \\ g & 0 \end{pmatrix}$$

$$\underline{R} = \underline{G}^{-1}$$

$$\det G = 0$$