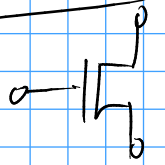


# ST 1 - Tutorübung - Blatt 8 (22.12.09)

## MOSFET-Schaltung

n-MOS



$U_{th} > 0V$   
"normally off"


n-MOS-Enhancement-Typ



$U_{th} < 0V$   
"normally on"

n-MOS-Depletion-Typ

p-MOS

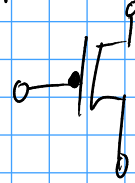

$U_{th} < 0$   
"normally off"

p-Kanal-Enhancement

Festlegung von Drain/Source:

$u_{ds} \geq 0V$

— " —  
 $u_{ds} \leq 0V$

Schaltungstheoretische: Shichman-Hodges-Modell

(hier: ohne Berücksichtigung der Kanal-längenmodulation)

n-MOS:  $i_g = 0$

$$i_d = \begin{cases} 0 & u_{gs} - U_{th} \leq 0 \\ \beta \left( (u_{gs} - U_{th}) u_{ds} - \frac{1}{2} u_{ds}^2 \right) & 0 \leq u_{gs} - U_{th} \leq u_{ds} \\ \frac{\beta}{2} (u_{gs} - U_{th})^2 & 0 \leq u_{gs} - U_{th} \leq u_{ds} \end{cases}$$

$$\left. \frac{\partial i_d}{\partial u_{gs}} \right|_{AP} = \frac{\beta}{2} \cdot 2(u_{gs} - U_{th}) \Big|_{AP} = \frac{A}{V^2} \cdot V = \frac{A}{V} = S$$

p-MOS:

$$i_g = 0$$

$$i_d = \begin{cases} 0 & u_{gs} - U_{th} \geq 0 \\ -\beta (u_{gs} - U_{th}) u_{ds} - \frac{1}{2} \beta u_{ds}^2 & 0 \leq u_{gs} - U_{th} < u_{ds} \\ -\frac{\beta}{2} (u_{gs} - U_{th})^2 & 0 \geq u_{gs} - U_{th} \geq u_{ds} \end{cases}$$


$$\begin{aligned} & 0 \leq u_{gs} - U_{th} < u_{ds} \\ & 0 \geq u_{gs} - U_{th} \geq u_{ds} \end{aligned}$$

### Merleitung der KS-ESBs:

z.B. n-MOS-Schaltung, linearer Bereich


neu!

$$\left. \begin{aligned} \frac{\partial i_d}{\partial u_{ds}} \Big|_{AP} &= \beta [(u_{gs} - U_{th}) - u_{ds}] \Big|_{AP} = \beta [(U_{gs} - U_{th}) - U_{ds}] \\ \frac{\partial i_d}{\partial u_{gs}} \Big|_{AP} &= \beta u_{ds} \Big|_{AP} = \beta U_{ds} \end{aligned} \right\} \begin{array}{l} \text{ausgehend} \\ \text{von den} \\ \text{Stromman-} \\ \text{Modges-Glei-} \\ \text{chungen} \end{array}$$


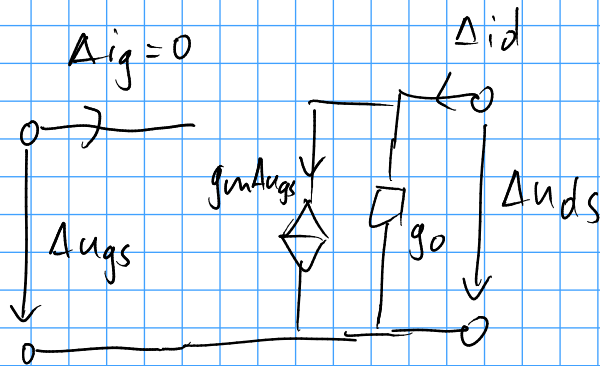


Kleinsignal-ESB für den linearen Bereich

→ Analog: Sättigungsbereich

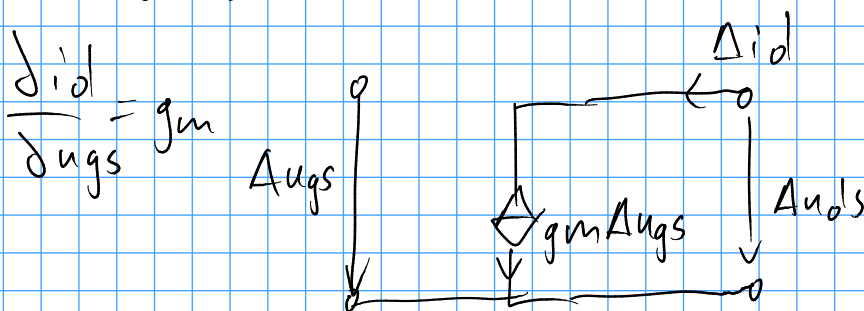

# Aufgabe 1 :

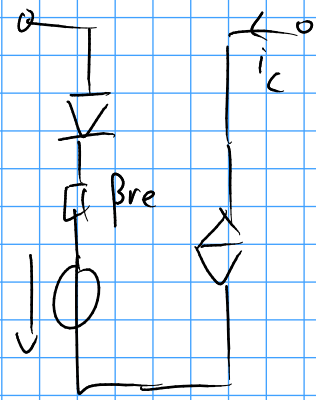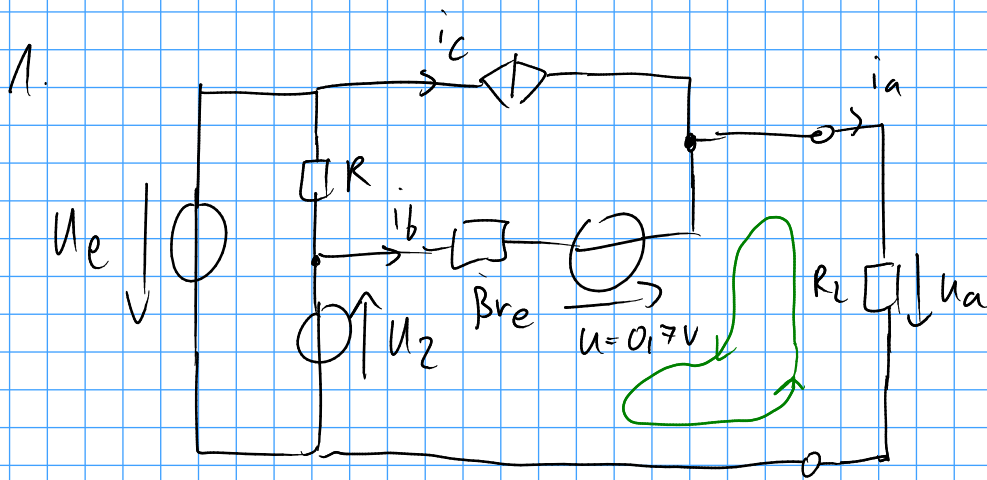

2.  $R_L = \frac{U_a}{I_a}$

3.  $I_a = f(I_b, \beta)$

$$I_a = I_b + I_c = I_b + I_b \beta = I_b (\beta + 1)$$

4.  $I_b = \frac{I_a}{(\beta + 1)} = \frac{U_a}{R_L (\beta + 1)}$  (aus (2) u. (3))

5.  $U_a = f(U_2, \beta, R_L, r_e)$

$$U_a = -U - \beta r_e I_b - U_2 = -U - \beta r_e \frac{U_a}{R_L (\beta + 1)} - U_2$$

$$U_a \left( 1 + \frac{\beta r_e}{R_L (\beta + 1)} \right) = -U - U_2 = -0.7V - U_2 \quad | : (\sim)$$


$$U_a = \frac{-0.7V - U_2}{1 + \frac{\beta r_e}{R_L (\beta + 1)}}$$

$$6. \lim_{r_e \rightarrow 0} U_a = -0,7V - U_2$$

7. → spannungsgesteuert

→ passiv


→ quellenfrei

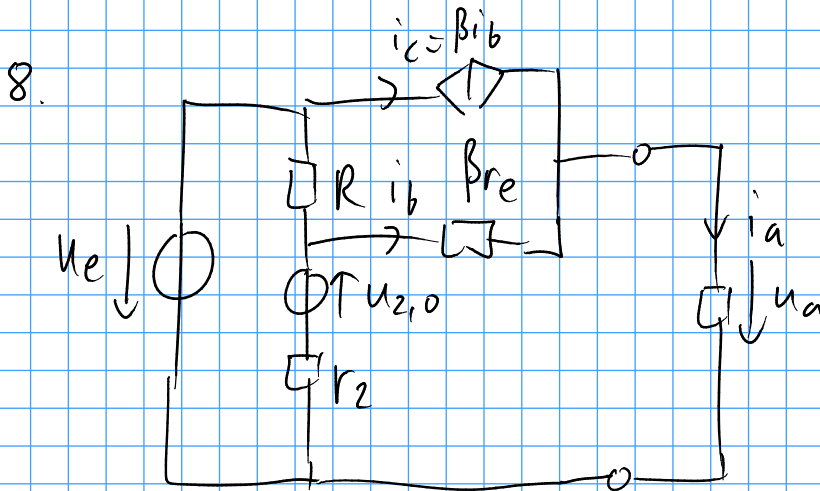

$$r_2 = \frac{1}{7} k\Omega$$

$$U_{2,0} = -6,07V$$

Kleinsignal-Analyse

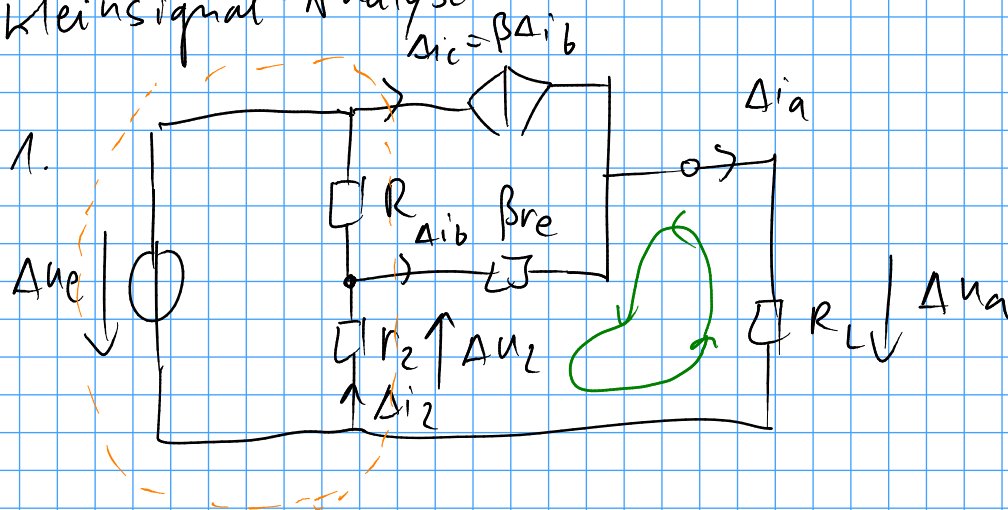

$$2. \Delta U_a = f(\Delta U_2, \beta, R_L, r_e) \quad ; \quad \Delta i_a = \Delta i_b (\beta + 1) \quad R_L = \frac{\Delta U_a}{\Delta i_a}$$

$$\Delta U_a = -\beta r_e \Delta i_b - \Delta U_2 = -\beta r_e \frac{\Delta U_a}{R_L (\beta + 1)} - \Delta U_2$$

$$\Delta u_a \left( 1 + \frac{\beta r_e}{R_L(\beta+1)} \right) = -\Delta u_2 \quad | : (-)$$

$$\Rightarrow \Delta u_a = \frac{-\Delta u_2}{1 + \frac{\beta r_e}{R_L(\beta+1)}}$$

$$3. \Delta i_b = 0 \Rightarrow \Delta u_2 = f(\Delta u_e, R, r_2)$$

$$\Delta u_2 = -\Delta u_e \frac{r_2}{R+r_2}$$

$$\Delta u_a = + \frac{1}{1 + \frac{\beta r_e}{R_L(\beta+1)}} \Delta u_e \frac{r_2}{R+r_2}$$